Pierre-Antoine Graham

Homework 2

Eduardo Martín-Martínez, Bindiya Arora Quantum Information

Contents

1	Back to basics: quantum circuits	2
2	Quantum Adder	3
3	Grover's algorithm on IBM composer	2
4	Acknowledgement	_

Back to basics: quantum circuits

In what follows, we evaluate the matrix expressions representing a quantum circuit unitary acting on a sequence of qubit input. We work in the computational basis $\{|0\rangle, |1\rangle\}$ and use the notation X, Y, Z for the Pauli gates in this basis.

(a) First we consider the conjugation of a CNOT by two CNOT with control and target qubit reversed:

which exchanges the qubits $(|00\rangle \rightarrow |00\rangle, |01\rangle \rightarrow |10\rangle, |10\rangle \rightarrow |01\rangle, |11\rangle \rightarrow |11\rangle)$ and constitutes a SWAP gate. The matrix expression for the reversed CNOT was obtained by writing its action on the computational basis which reads $|00\rangle \rightarrow |00\rangle, |01\rangle \rightarrow |11\rangle, |10\rangle \rightarrow |10\rangle, |11\rangle \rightarrow |01\rangle$.

(b) Then we calculate the matrix expression of the entanglement-generating circuit

$$\begin{array}{l} 1 \\ 2 \\ \hline H \\ \hline \\ R_{\pi/4} \\ \hline \\ = (1_1 \otimes |0\rangle \langle 0|_2 + X_1 \otimes |1\rangle \langle 1|_2) \\ R_{\pi/4,2} \bigg(1_1 \otimes \frac{1}{\sqrt{2}} (X_2 + Z_2) \bigg) \\ = (1_1 \otimes |0\rangle \langle 0|_2 + X_1 \otimes e^{i\pi/4} |1\rangle \langle 1|_2) \bigg(1_1 \otimes \frac{1}{\sqrt{2}} (X_2 + Z_2) \bigg) \\ = \frac{1}{\sqrt{2}} \bigg(1_1 \otimes |0\rangle_2 (\langle 0|_2 + \langle 1|_2) + X_1 \otimes e^{i\pi/4} |1\rangle_2 (\langle 0|_2 - \langle 1|_2) \bigg) = \frac{1}{\sqrt{2}} \bigg(\begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} \otimes \begin{pmatrix} 1 & 1 \\ 0 & 0 \end{pmatrix} + \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \otimes \begin{pmatrix} 0 & 0 \\ e^{i\pi/4} & -e^{i\pi/4} \end{pmatrix} \bigg) \\ = \frac{1}{\sqrt{2}} \bigg(\begin{pmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 1 & 1 \\ 0 & 0 & 0 & 0 \\ e^{i\pi/4} & -e^{i\pi/4} & 0 & 0 \\ \end{pmatrix} = \frac{1}{\sqrt{2}} \bigg(\begin{pmatrix} 1 & 1 & 0 & 0 \\ 0 & 0 & e^{i\pi/4} - e^{i\pi/4} \\ 0 & 0 & 1 & 1 \\ e^{i\pi/4} & -e^{i\pi/4} & 0 & 0 \\ \end{pmatrix} \bigg).$$

If we set the phases to 1, we recover the Bell state mapping $|00\rangle \rightarrow (|00\rangle + |11\rangle)/\sqrt{2}, |01\rangle \rightarrow (|00\rangle - |11\rangle)/\sqrt{2}, |10\rangle \rightarrow (|01\rangle + |10\rangle)/\sqrt{2}$ and $|11\rangle \rightarrow (-|01\rangle + |10\rangle)/\sqrt{2}$.

(c) Finally, we calculate the matrix expression associated with a three-qubit circuit as follows:

2 Quantum Adder

(a) The TOFFOLI gate can be generalized to *n* qubits by increasing the number of control qubit to *n* − 1 conditioning a NOT operation on qubit *n*. The circuit corresponding to this generalisation is presented in Fig. 1 (a).



(a) n-qubit generalisation of the TOFFOLI gate.

(b) Circuit for the addition of two single bit numbers a and b.

Figure 1: Circuits for 2 (a) and 2 (b).

- (b) Given two single digit binary numbers a and b, we can calculate a + b with a quantum circuit by encoding them in input numbers in qubit states |a⟩ and |b⟩ where the digit forms the 0,1 label of a computation basis element. In other words, the classical bit adder algorithm can be implemented with a quantum circuit. This algorithm requires qubits for inputs a and b and a qubit initialized to |0⟩ that will eventually be updated to store the carry on of a + b (if we add 1+1 we get 10 which is represented here by having 1 stored in the carry on qubit, and 0 stored in the output state for the b qubit hilbert space. The state of a is unchanged to allow for reversibility of calculation and its implementation as a sequence of unitary operations). The Quantum circuit implementing the single is presented in Fig. 1 (b). On one hand the TOFFOLI gate flips the carry on c to 1 iff both a and b are initialized to 1. On the other hand the CNOT gate replaces the value of b by a XOR b storing the first digit of the adition output in b.
- (c) If we consider adding 4 binary numbers a, b, c, d together, we need an additional carry on qubit to represent the result since 1+1+1=100 requires 3 qubits to describe its digits. In this case we name the carry on c_1 and c_2 . The circuit performing the addition of 4 single bit numbers together is presented in Fig. 2 The first two layers of this circuit add a and b in the way explained in (b). At the

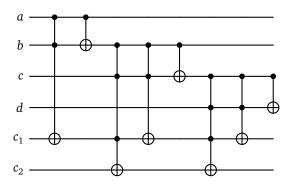


Figure 2: Circuit for the addition of four single bit numbers a, b, c, d. The output is stored in qubit d (first digit), c_1, c_2 (last digit)

second layer the CNOT operation shifts the last digit output to the b qubit. The next group of operations uses the value stored in b,c,c_1 to add the updated b and c while taking the c_1 carry on into account. The first gate of the third layed flips c_2 iff b,c,c_1 are all one (in our case this does not happen because $c_1=0$ implies b=0). The fourth and fifth layers are copies of the operations described in (b) acting on b,c,c_1 . At the fifth layer, the CNOT operation shifts the last digit output to the c qubit. At layer six, a generalised TOFFOLI is applied to possibly flip the c_2 carry on if c,d,c_1 are all 1 (which is a real possibility in this case). The seventh layer updated the value of the c_1 carry on from the values of c,d (if it was 1 and gets a 1 contribution from c,d, it is flipped to 0. The requiered carry on to c_2 associated with this flip was allready done by the sixth layer). At the last layer the CNOT operation shifts the last digit output to the d qubit. The final output of the addition is stored in qubits d,c_1,c_2 .

- **3** Grover's algorithm on IBM composer
- 4 Acknowledgement